

The very first step our team took was to divide the entire circuit into a few subparts. After careful analysis, the circuit was split into three major parts: The bias circuit, the folded cascode stage, and the common source stage. The gain was entirely determined by the folded cascode and the CS stages. And the bias circuit acted like a voltage and current source that was used to bias the folded cascode stage and the common source stage.


Our team put our focus on the folded cascode and common source stages first. The role of the bias circuits was replaced by a bunch of ideal voltage sources first. We first calculated some node voltages that required the bias voltage sources such as the nodes between M4a and M4b, the node between M5a and M5b, and the node between M6a and M6b. We assumed some appropriate overdrive voltages for the transistors and calculated some other key node voltages with the knowns. We also picked a value in the input common mode range to run the nominal test. We did not expect a large gain as the large gain would mess up the unity bandwidth. Since the folded cascode tended to provide more gain, our team split the gain to 50dB for the folded cascode stage and 20 dB for the CS stage to reach the requirement of 70dB.

Next we tried to locate the positions of the dominant pole and non-dominant pole to meet the constraints of the phase margin, gain margin, and unity gain bandwidth. We tried to push the dominant pole as close as to the imaginary axis and we also know that the frequency of the non-dominant pole is much larger than the dominant pole. Another insight was that C_c will give a rise to the zero so that a means to mitigate the zero's effect is necessary. We can either push the zero further away to the infinity or we can cancel out the zero with the non-dominant pole, the one who has a major effect on phase margin, by determining the value of the R_c .


For the design of the bias circuit, our team decides to construct the circuit from right to left towards the constant g_m part. We set the current quite small in order to meet the power constraint. The key parts in the bias circuit were the nodes that led to bias the folded cascode and CS circuits. Our main goal here was to set those nodes to the voltages that we were used to bias the folded cascode and CS circuit so that those stages could function properly just as we used the ideal voltage sources to bias them. We also noticed that since most of the transistors in the bias circuit were either current mirrors and diodes connected, they should all be in saturation except for Mb5b and Mb14b. Also we kept $m < 20$ in the constant g_m circuit. Another crucial step was to first estimate the gate voltage between Mb8 and Mb11 and bias that node to fulfill the desired node voltages at Mb6 and Mb15 which biased the two stages. So what we needed to do was to construct a constant g_m circuit that can provide a voltage at the gate Mb3 that led to the node between Mb8 and Mb11 so that the same results could be obtained.

Schematic of our final design with component values


Size of two stages amplifier

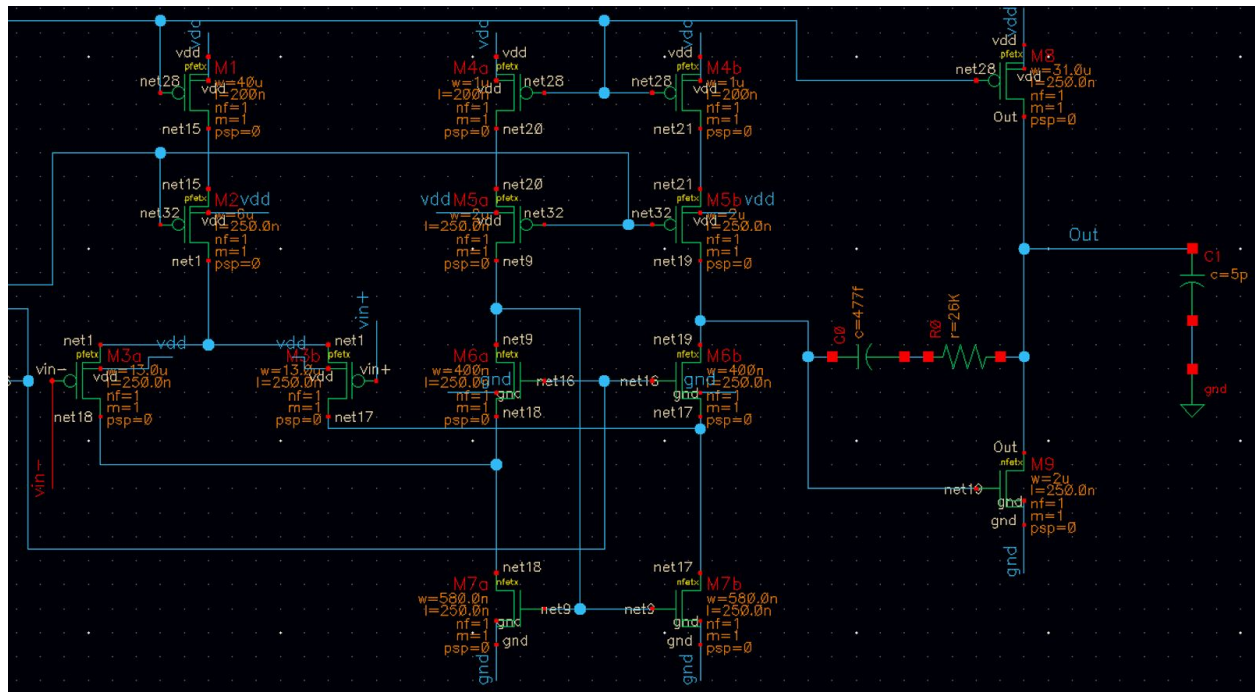


Size of bias circuit

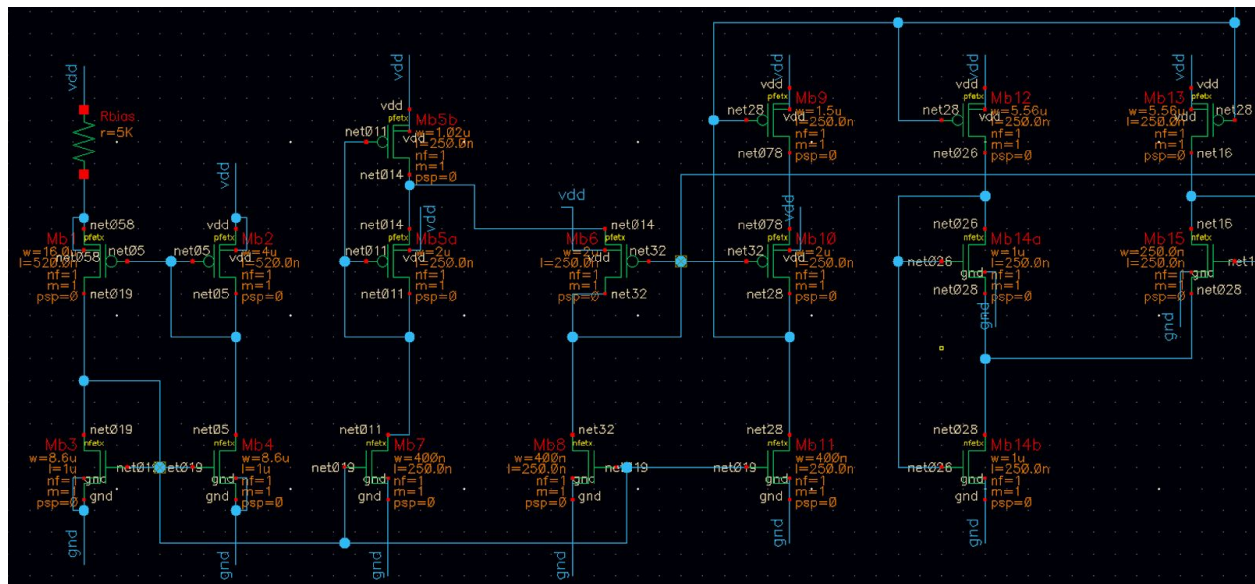

Operation point of two stages amplifier

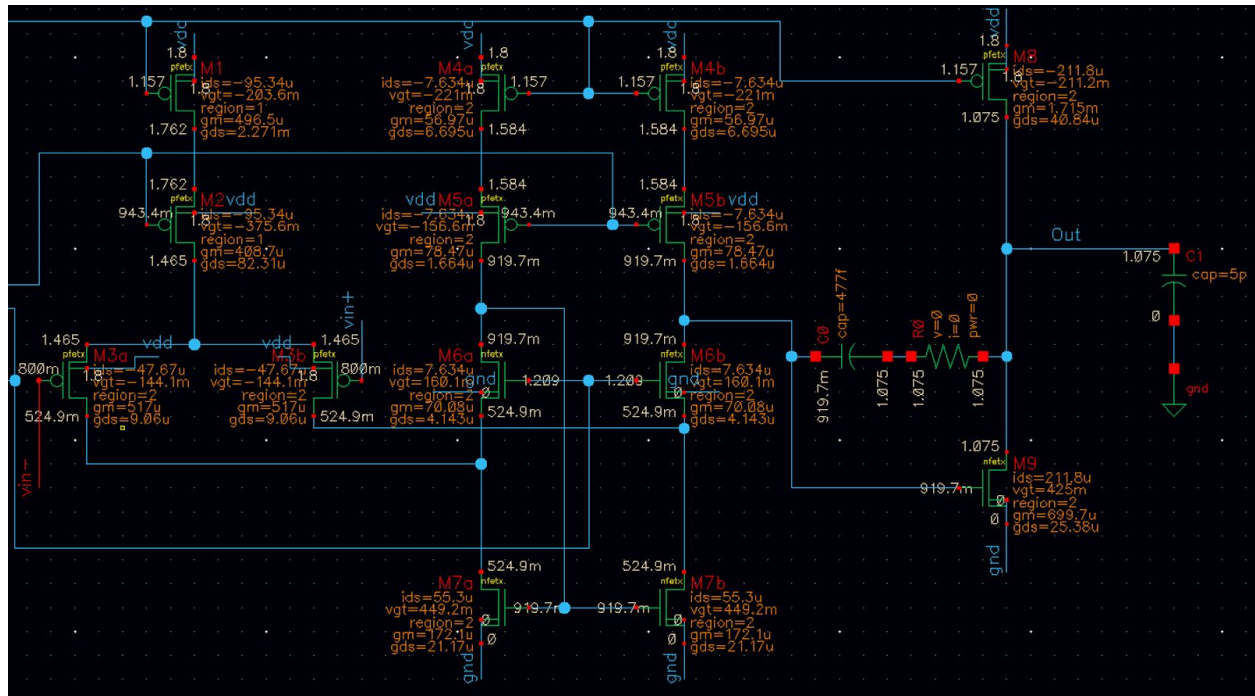

Operation point of bias circuit

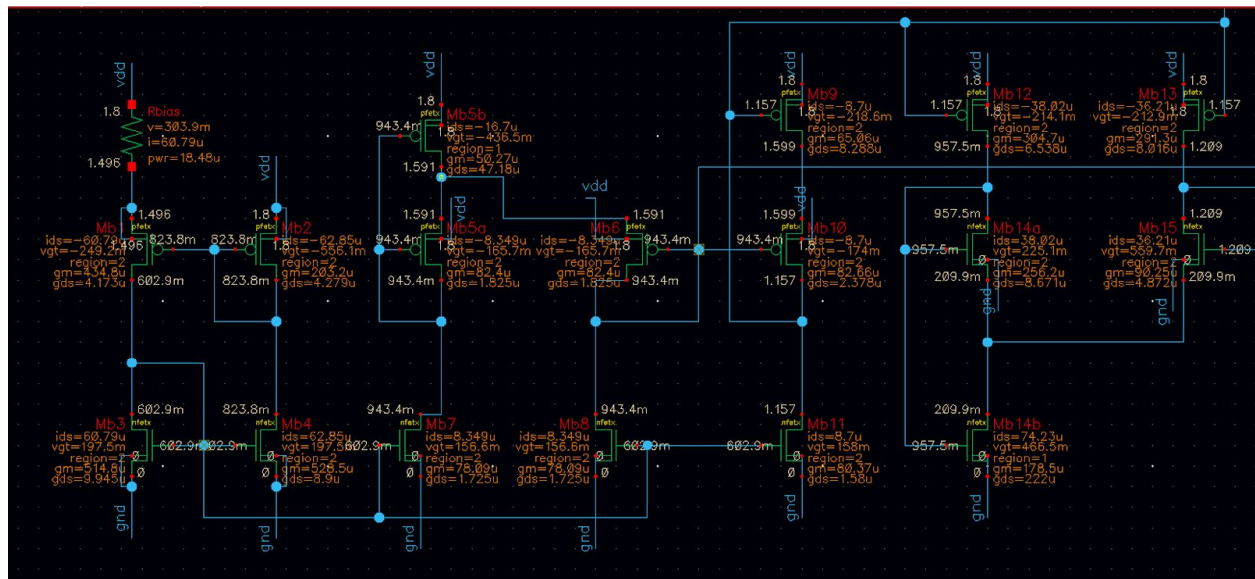

Calculation part

Some technology parameters:

$$K_n' = 260\mu A/V^2 \quad \lambda = 0.1$$

$$K_p' = 50\mu A/V^2 \quad |V_{tp}| = 383mV$$

if we consider back gate effect, V_{tn} and V_{tp} will increase, so we assume:

$$V_{tn} = 400mV, \quad V_{tp} = 450mV$$

The gain of folded cascode:

$$R_{out} = r_{o5} (1 + g_{m5} r_{o4b}) \parallel r_{o6b} (1 + g_{m6b} (r_{o7b} \parallel r_{o3b})) \quad \text{if } g_{m6} > > 1$$

$$\text{We have: } R_{out} = g_{m5} r_{o5} r_{o4b} \parallel g_{m6b} r_{o6b} (r_{o7b} \parallel r_{o3b})$$

$$A_v = g_{m3} R_{out}$$

The gain of CS:

$$A_v = g_{m9} (r_{o8} \parallel r_{o9})$$

First, we analyzed the folded cascode and determine the bias voltages where we put the ideal voltage sources at.

For $M_{3a,b}$ in saturation, we first set $V_{g3} = V_{en} = 0.8V$ and $v_{ds3} = 0.15V$ to make M_1, M_2 easier in saturation.

$$V_{ds3} = V_{S3} - 0.8 - V_{tp}$$

$$V_{S3} = V_{ds3} + 1.25 = 1.4V = V_{D2}$$

For M_2 , set $v_{ds2} = 0.2V, \quad V_{D2} = 0.2V$.

$$V_{S2} = 0.2 + V_{D2} = 1.6V = V_{D1}$$

$$V_{G2} = V_{S2} - V_{ds2} - V_{tp} = 1.6 - 0.2 - 0.45 = 0.95V$$

For M_1 : assume $V_{ov1} = 0.2V, \quad V_{SD1} = 0.2V$.

$$V_{S1} = 0.2 + V_{D1} = 1.8V$$

$$V_{G1} = 1.8 - 0.2 - 0.45 = 1.15V$$

For M_5 : $V_{g5} = 0.95V$. assume $v_{ds5} = 0.2V$.

set $V_{D5} = 0.95V$ this is also the gate voltage of M_9 also the gate of M_7 $V_{ov7} = 0.95 - 0.4 = 0.55V$.

$$V_{DS7} > V_{ov7} \Rightarrow V_{D7} \approx V_{S6} \geq V_{ov7} = 0.55V$$

I choose $V_{S6} = 0.6V$.

For M_6 : $V_{ov6} = 0.2V$

$$V_{g6} = V_{S6} - V_{tn} = 0.2$$

$$V_{g6} - V_{S6} = 0.6V$$

$$V_{g6} = 1.2V$$

I then chose these three voltages to bias the folded cascode and CS.

Frequency analysis.

For M_q : $V_{ov} = V_{gs} - V_t = 0.95 - 0.4 = 0.55V$

The total gain of this circuit is $70dB = 3162$

To achieve the Unity GBW $\geq 100MHz$ we have:

$$W_c = W_{p1} A_v$$

$$f_{p1} = \frac{W_c}{A_v} = \frac{2\pi \cdot 10^8}{3162} \approx 2 \times 10^5 \text{ Hz}$$

We know f_{p2} is much larger than f_{p1} so let's assume it to be 10^8 Hz

We also have: $f_{p2} = \frac{g_{m9}}{C_L} \Rightarrow 10^8 = \frac{g_{m9}}{5 \times 10^{-12}} \Rightarrow g_{m9} = 5 \times 10^{-4} S$

$$I_8 = I_9 = \frac{g_{m9} V_{ov9}}{2} = 1.375 \times 10^{-4} A = 137.5 \mu A$$

$$\left(\frac{W}{L}\right)_9 = \frac{137.5 \times 2}{260 \times 0.55^2} \approx 3.5$$

Assume $V_{ov9} = 0.2V$

$$\left(\frac{W}{L}\right)_8 = \frac{137.5 \times 2}{50 \times 0.2^2} = 137.5$$

For folded Cascode.

$$A_v = g_{m3} R_{eq}$$

$$R_{eq} = g_{m56} r_{o56} r_{o4b} \parallel g_{m66} r_{o66} (r_{o7b} \parallel r_{o3b})$$

$$= \frac{2I_5}{V_{ov5}} \cdot \frac{1}{\lambda I_5} \cdot \frac{1}{\lambda I_5} \parallel \frac{2I_5}{V_{ov6}} \cdot \frac{1}{\lambda I_5} \left(\frac{1}{\lambda I_7} \parallel \frac{1}{\lambda I_3} \right)$$

Assuming $V_{ov5} = V_{ov6} = 0.2V$.

$$A_v = \frac{2I_3}{V_{ov3}} \cdot \frac{2}{V_{ov5} \lambda^2 (2I_5 + 2I_3)}$$

where $V_{ov3} = 0.15V$, $V_{ov5} = 0.2V$, $\lambda = 0.4$ (nmos λ is larger than 0.1)

$$2.3 \approx 3I_5$$

Assume $I_{4+6} = 10 \mu A$, $I_3 = 30 \mu A$, $I_7 = 10+30 = 40 \mu A$, $I_{1,2} = 80 \mu A$.

$$g_{m4,5,6} = \frac{2I}{V_{ov}} = 100 \mu S$$

$$g_{m7} = \frac{2I}{V_{ov}} = 145 \mu S$$

$$g_{m3} = \frac{2I}{V_{ov}} = 300 \mu S$$

$$g_{m1,2} = \frac{2I}{V_{ov}} = 200 \mu S$$

$$g_{m8} = \frac{2I}{V_{ov}} = 1.375 mS$$

$$g_{m9} = \frac{2I}{V_{ov}} = 500 \mu S$$

$$\left(\frac{W}{L}\right)_{4,5} = 10 = \frac{2.5 \mu A}{250 n}$$

$$\left(\frac{W}{L}\right)_6 = 2 = \frac{250 n}{250 n}$$

$$\left(\frac{W}{L}\right)_7 = 1 = \frac{250 n}{250 n}$$

$$\left(\frac{W}{L}\right)_3 = 30 = \frac{7.5 \mu A}{250 n}$$

$$\left(\frac{W}{L}\right)_{2,1} = 60 = \frac{15 \mu A}{250 n}$$

the actual values are adjusted to meet the constraints such as $V_{ov} \geq 50mV$, gain $\geq 70dB$, etc.

Bias circuit:


We decided to the bias circuit from right to left.

Notice that the current through $M_2 / M_4 / M_1$ are all mirrored from the current through M_{b9} with different m factors. So I set the current through M_{b12}, M_{b13} to be $40\mu A$ in order to keep the power small.

The final $I_{q,8}$ I got from my CS stage is $144\mu A$, so for $I=40\mu A$ for M_{b12} , I should make $\frac{W}{L}$ smaller assuming V_{ov} is the same with the value of $0.2V$.

$\therefore \frac{W}{L} M_{b12}, M_{b13}$ is $\left(\frac{40}{144} \cdot \frac{W}{L}\right)_8 = \frac{5.56\mu}{250n}$ and for M_{b14} , and M_{b15} , since they are nmos with larger k_n' , I set their $\left(\frac{W}{L}\right)$ to be $\frac{1\mu}{250n}$ for convenience reason. I also keep $\left(\frac{W}{L}\right)_{b4b}$ as $\frac{1\mu}{250n}$, notice it's in triode.

 for M_{b9}, b_{10}, b_{11} Initially I set the current the same as $40\mu A$. So I got $\left(\frac{W}{L}\right)_{b9/10} = \frac{5.56\mu}{250n}$ and $\left(\frac{W}{L}\right)_{b11} = \frac{1\mu}{250n}$. The key part here is to calculate a bias voltage between gate of M_{b8} and M_{b11} .



For M_{b11} :

$$V_{g11} - 0 - 0.4 = 0.2$$

$$V_{g11} = 0.6V$$

So I bias this gate with $0.6V$ for now. Here I tried to make the node between M_{b6}, M_{b10} to be $0.95V$ and the gate of $M_{b15} = 1.2V$ with only one bias source at gate of $M_{b12}, b_{12}, b_{13} = 1.15V$.

$$\left(\frac{W}{L}\right)_{b6, b5b} = \frac{5.56\mu}{250n} \quad \left(\frac{W}{L}\right)_{b8, b7} = \frac{1\mu}{250n}$$

$$\left(\frac{W}{L}\right)_{b5a, b6b} = \frac{2.7\mu}{250n}$$

Next step is to construct constant gm which achieve the node voltage between $M_{b3,4} = 0.6V$. Initially I assume current is $40\mu A$. I chose $m=4$

$$I_d = \frac{V_{ovb2} \left(1 - \frac{1}{\sqrt{4}}\right)}{R_2} \quad \text{where } V_{ov2} = 0.2 \quad I_d = \frac{1}{2} k_n' \frac{W}{L} V_{ov}^2$$

$$\frac{W}{L} = \frac{100}{13}$$

$$R_2 = 5k\Omega$$

I use $\left(\frac{W}{L}\right)_{b2} = \frac{4\mu}{550n}$ So that $\left(\frac{W}{L}\right)_{b1} = \frac{16\mu}{550n}$ Then I did dc sweep at that node to select a $\left(\frac{W}{L}\right)_{b3,4}$ to provide a $0.6V$ voltage at gate of $M_{b3,4}$. $\left(\frac{W}{L}\right)_{b3,4} = \frac{8.6\mu}{1\mu}$

After everything was set, I put all parts together and discard the $1.15V$ ideal voltage source and tweak around the $\left(\frac{W}{L}\right)$ of all transistors to achieve the requirement of all $V_{ov} \geq 150mV$ and achieve the gate of $M_{b9,12,13}$ to have $1.15V$, gate of $M_{b6,10}$ to have $0.95V$, and gate of M_{b15} to have $1.2V$.

Power dissipation:

$$P = I \cdot V = (137.5 + 10 \times 2 + 60 + 40 \times 5 + 80) \times 10^{-6} \times 1.8 = 895 \mu W. < 2.5 mW$$

Some key parameter comparison:

parameters:	Hand Calculations	SPICE values:
$I_{B,9}$	137.5 μ A	121.8 μ A
$I_{A,5,6}$	10 μ A	7.634 μ A
I_7	40 μ A	55.3 μ A
I_3	30 μ A	47.67 μ A
$I_{1,2}$	60 μ A	95.34 μ A
g_{m9}	500 μ S	699.7 μ S
g_{m8}	1.375 μ S	1.715 μ S
g_{m7}	145 μ S	172 μ S
$g_{m A,5,6}$	100 μ S	56.9 μ S, 78.47 μ S, 70.08 μ S
g_{m3}	200 μ S	517 μ S
$g_{m1,2}$	200 μ S	496 μ S, 408 μ S
C_C	477 fF	477 fF
R_C	23 k Ω	26 k Ω
Power Dissipation	895 μ W	982.2 μ W


Reasons of Discrepancies:

For currents, the discrepancies were actually quite small. The reason that these discrepancies exist might be in reality, I_d are actually experiencing CLM while when I first estimated the values, I did not take that into account for convenience. And g_m values are little off because first I_s are different and second, v_{ov} are not the ones we assumed.

R_C , R_C are adjusted to meet phase margin / gain margin requirements but overall are constant. Power is little bit more because the actual currents amount is larger because of CLM.


Bode plot simulation results

Gain and Phase Margin

 


Phase Margin by calculation: 73.4 degree(approximately the same)

DC gain

 

 Transient simulation results for a 10 μVpp sinusoid at 20 kHz.



Result of Test Bench showing Unity Gain Bandwidth and Power.

Outputs				
	Name/Signal/Expr	Value	Plot	Save
2	Gain Margin	-16.51	<input checked="" type="checkbox"/>	<input type="checkbox"/>
3	Phase Margin	71.45	<input checked="" type="checkbox"/>	<input type="checkbox"/>
4	Unit gain BW	200.7M	<input checked="" type="checkbox"/>	<input type="checkbox"/>
5	Phasd	wave	<input checked="" type="checkbox"/>	<input type="checkbox"/>
6	dc gain	70.35	<input checked="" type="checkbox"/>	<input type="checkbox"/>
7	power	982.2u	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>

Conclusion:

This is definitely a challenging project for us but also a valuable experience especially for those who later would go into the industry.

We have learned tons of useful information and steps that are required for solving such a practical problem. First of all, we have learned that before starting to solve a problem, we should first divide the problem into small blocks and decide which parts should be our priority and most critical. On the top of that, we have learned how to integrate the knowledge we learned from the lectures and homework into solving this project. We now know how to make proper and educated estimations to give us a starting point to solve an intricate circuit. The most challenging part came when we tried to determine the current ratio between I3 and I5. We kept getting the wrong results until we found out that λ actually made a huge impact on the results. From this experience, we learned that any small seemingly trivial values can make a huge difference. We basically need to take anything into consideration. We also gain a deeper understanding on poles and zeros and how they impact the design.